

① At an operating frequency of 500 M rad/s, typical. ①

Circuit values for a certain transmission line are $R = 0.2 \Omega/m$

$L = 0.25 \mu H/m$, $G = 10 \mu S/m$ and $C = 100 \text{ pF}/m$ find

② α ③ β ④ V_p ⑤ λ ⑥ Z_0

$$\rightarrow Z = R + j\omega L, Y = G + j\omega C = 10 \times 10^{-6} + j500 \times 10^6 \times 100 \times 10^{-12}$$
$$= 0.2 + j500 \times 10^6 \times 0.25 \times 10^{-6}$$

$$Z = 0.2 + j125 = 125 \angle 89.9^\circ$$

$$Y = 10 \times 10^{-6} + j0.05 = 0.05 \angle 89.99^\circ$$

$$Y = \sqrt{ZY} = 0.0024 \angle 178.89^\circ 2.5 \angle 89.945^\circ$$

$$= 0.0024 + j2.5$$

$$\alpha = 0.0024 \text{ Np/m} \quad \beta = 2.5 \text{ rad/m.}$$

$$V_p = \frac{\omega}{\beta} = \frac{500 \times 10^6}{2.5} = 2 \times 10^8 \text{ m/s.}$$

$$\lambda = \frac{V_p}{f} = \frac{2 \times 10^8 \times 2\pi}{500 \times 10^6} = \frac{4\pi}{5} = 2.513 \text{ m.}$$

$$Z_0 = \sqrt{\frac{Z}{Y}} = 50 \angle -0.045^\circ = 49.99 - j0.03927 \Omega$$

② Suppose an transmission line is probed and it is found that the distance between minima is 2cm. The minima position does not shift when the actual

load is replaced by a short circuit. The standing wave ratio of unknown load is 2. What is the load impedance and operating frequency. (Propagating mode is TEM). Characteristic impedance of the line be 50Ω .


$$\rightarrow \frac{\lambda}{2} = 2\text{cm} \Rightarrow \lambda = 4\text{cm}$$

$$\Rightarrow f = \frac{c}{\lambda} = \frac{3 \times 10^8}{4 \times 10^{-2}} = \frac{3}{4} \times 10^{10} = 7.5 \text{ GHz.}$$

$$Z_{\text{normalised}} = 0.5$$

$$Z_L = 0.5 \times 50 = 25\Omega$$

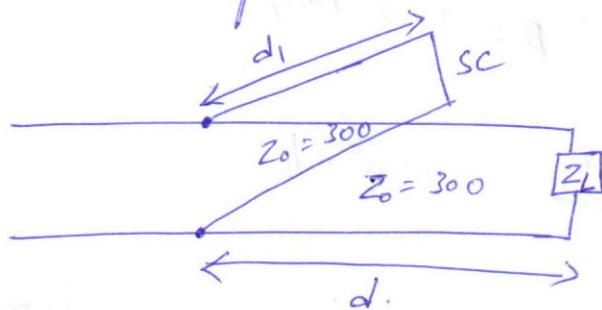- ③ The lossless line shown in the figure is operating with $\lambda = 100\text{cm}$. If $d_1 = 10\text{cm}$, $d = 25\text{cm}$ and the line is matched to the left of the stub. What is Z_L ?



Case① $d = 25\text{cm}$.

Case② $d = 20\text{cm}$.

- ④ A series of measurements are made on a line using an impedance bridge. All measurements are made at the same point on the line. First the input impedance with the unknown load impedance in place is measured as.

$Z_{\text{in}} = 30 + j60 \Omega$. Since the line is not marked its characteristic resistance is not known. So the load is replaced by a short circuit and the input

(2)

impedance is measured as $Z_{in}^{sc} = j53.1 \Omega$. Repeating the procedure with the load replaced by an open circuit gives $Z_{in}^{oc} = -j48.3 \Omega$. Find Z_0 & Z_L .

$$Z_0 = \sqrt{Z_{sc} Z_{oc}} = \sqrt{j53.1 \times -j48.3} = 50.643 \Omega$$

$$Z_{in} = Z_0 \left[\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right]$$

$$= Z_0 \left[\frac{Z_L \cos \beta l + jZ_0 \sin \beta l}{Z_0 \cos \beta l + jZ_L \sin \beta l} \right]$$

$$= Z_0 \frac{\cos \beta l}{\sin \beta l} \left[\frac{Z_L + jZ_0 \tan \beta l}{Z_0 \cot \beta l + jZ_L} \right]$$

$$= -jZ_0 \cot \beta l \left[\frac{Z_L + jZ_0 \tan \beta l}{-jZ_0 \cot \beta l + Z_L} \right]$$

$$= Z_{oc} \left[\frac{Z_L + Z_{sc}}{Z_L + Z_{oc}} \right]$$

$$Z_L = Z_{oc} \left[\frac{Z_{sc} - Z_{in}}{Z_{in} - Z_{oc}} \right] = -j48.3 \left[\frac{j53.1 - 30 - j60}{30 + j60 + j48.3} \right]$$

$$= 11.634 + j6.3 \Omega$$

- ⑤ A transmission line has $R = 15 \Omega/m$, $L = 2 \text{H/m}$, $C = 0.15 \times 10^{-6} \text{F/m}$, $G = 1 \times 10^{-6} \Omega^{-1}\text{m}$. Find the additional inductance to give a distortionless line. Also find the propagation constant at 1 kHz.

$$\rightarrow \frac{R}{L_1} = \frac{G_1}{C} \Rightarrow \frac{15}{L_1} = \frac{1 \times 10^{-6}}{0.15 \times 10^{-6}} \Rightarrow L_1 = 2.25$$

$$L_{ad} = L_1 - L = 2.25 - 2 = 0.25 \text{ H/m}$$

$$Y = \sqrt{(R+j\omega C)(G+j\omega C)} \quad \text{since } \frac{R}{L} = \frac{G}{C}$$

$$= R \sqrt{\frac{C}{L}} + j\omega \sqrt{LC}$$

$$\alpha = R \sqrt{\frac{C}{L}} = 15 \sqrt{\frac{0.15 \times 10^{-6}}{2.25}} = 3.83 \times 10^{-3} \text{ NP/m.}$$

$$\beta = \omega \sqrt{LC} = 2\pi \times 10^{+3} \sqrt{2.25 \times 0.15 \times 10^{-6}} \\ = 3.65 \text{ rad/m.}$$

⑥ A lossless line having an air dielectric has a characteristic impedance z_0 of 200Ω . The line is operating at 200 MHz and input impedance $Z_{in} = (200-j200) \Omega$. Use analytic method and the Smith chart to find.

(a) Input impedance, admittance.

(b) Input VSWR.

(c) Load impedance if the line is ~~1m long~~.

(d) VSWR at the load.

(e) The distance from the load to nearest voltage maximum.

$$\rightarrow (a) Y_{in} = \frac{1}{200-j200} = 2.5 \times 10^{-3} + j2.5 \times 10^{-3} \text{ S}$$

$$(b) \Gamma_{in} = \frac{Z_{in}-z_0}{Z_{in}+z_0} = \frac{200-j200-200}{200-j200+200} = 0.2-j0.4$$

$$VSWR_{in} = \frac{1 + |\Gamma_{in}|}{1 - |\Gamma_{in}|} = \frac{1 + 0.4472}{1 - 0.4472} = 2.61$$

(3)

$$\textcircled{c} \quad \lambda = \frac{3 \times 10^8}{200 \times 10^6} = \frac{3}{2} \text{ m}$$

$$\beta l = \frac{2\pi}{\lambda} l = \frac{2\pi}{3} \times 2 \times 1 = \frac{4\pi}{3} \approx 240^\circ$$

$$\textcircled{d} \quad Z_L = Z_0 \left[\frac{Z_{in} - jZ_0 \tan \beta l}{Z_0 - jZ_{in} \tan \beta l} \right] = 200 \left[\frac{200 - j200 - j200 \times \sqrt{3}}{200 - j(200 - j200) \sqrt{3}} \right]$$

$$= 226.24 + j211.09 \Omega$$

$$\textcircled{d} \quad \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{226.24 + j211.09 - 200}{226.24 + j211.09 + 200} = 0.447 \quad (56.56)$$

$$\textcircled{e} \quad VSWR_L = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + 0.447}{1 - 0.447} = 2.61$$


$$\textcircled{e} \quad 2P_{\text{max}} - \theta = 2\pi m \quad m = 0, 1, 2, 3, \dots$$

$m=0$, first maximum.

$$y_{\text{max}} = \frac{\theta}{2\beta}$$

$$= \frac{56.56 \times \pi}{180 \times 2 \times \frac{2\pi}{3} \times 2} = 0.117 \text{ m}$$

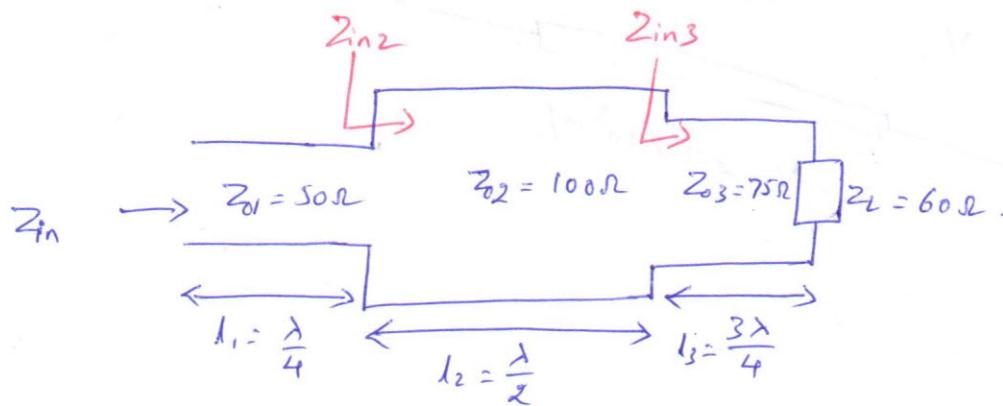\textcircled{f} Determine the input impedance.




$$Z_{in3} = \frac{75^2}{60} = 93.75 \Omega \rightarrow \text{Quater wave line.}$$


$$Z_{in2} = 93.75 \Omega \rightarrow \frac{\lambda}{2} \text{ line}$$

$$Z_{in} = \frac{\cancel{93.75} \Omega}{\cancel{93.75}} \frac{50^2}{93.75} = 26.67 \Omega \rightarrow \text{Quater wave line.}$$

Explanation
Quater wave line.

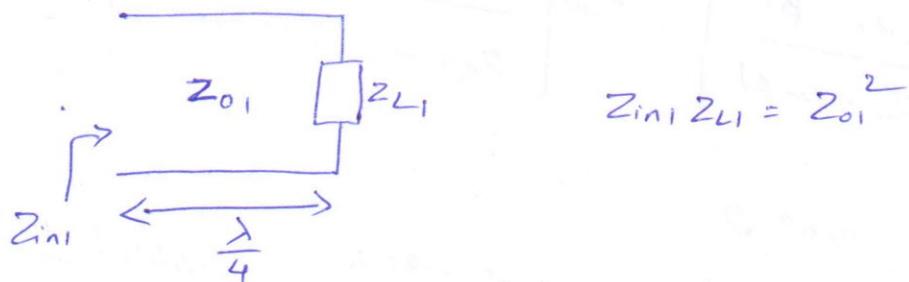


Half wave line

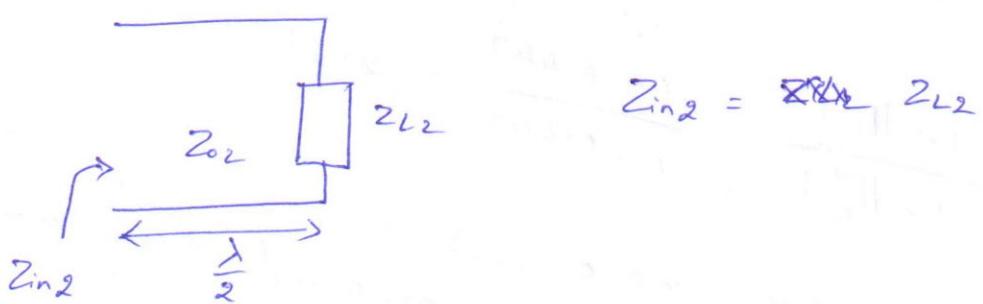


⑧ For the transmission line. Calculate ① V_{in} ② V_L ③ I_{in} ④ I_L

⑤ P_{in} ⑥ P_L

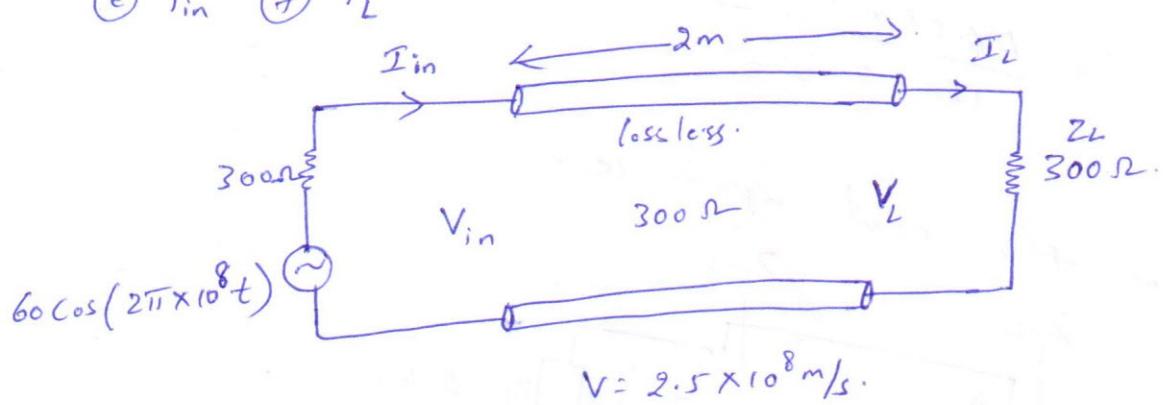

$$\rightarrow \left. \begin{array}{l} Z_L = 300 \Omega \\ Z_0 = 300 \Omega \end{array} \right\} \rightarrow Z_{in} = 300 \Omega$$

(4)

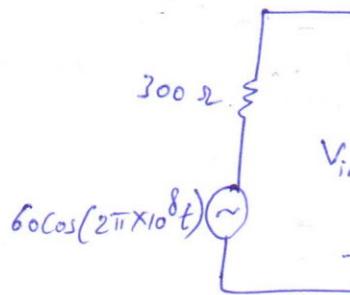

$$V_{in} = \frac{300}{600} 60 \cos(2\pi \times 10^8 t) \\ = 30 \cos(2\pi \times 10^8 t) V$$

Since $Z_L = Z_0$, there is no reflection and also line is lossless
therefore voltage at load is same as V_{in} but with delay
due to length of the line.

$$\beta l = \frac{2\pi}{\lambda} l = \frac{2\pi f}{\sqrt{V}} \times l = \frac{4\pi \times 10^8}{2.5 \times 10^8} = 1.6\pi \text{ rad.}$$

$$V_L = 30 \cos(2\pi \times 10^8 t - 1.6\pi) V$$

$$I_{in} = \frac{V_{in}}{Z_0} = 0.1 \cos(2\pi \times 10^8 t) A$$


$$I_L = \frac{V_L}{Z_0} = 0.1 \cos(2\pi \times 10^8 t - 1.6\pi)$$

$$P_{in} = \frac{1}{2} V_{in} I_{in} = \frac{1}{2} \times 30 \times 0.1 = 1.5 W$$

$$P_L = 1.5 W$$

⑨ A 70Ω lossless line has $s=2$ and $\theta_r = 200^\circ$. If the line is 0.3λ long obtain. ① Γ ② Z_L ③ Z_{in} .

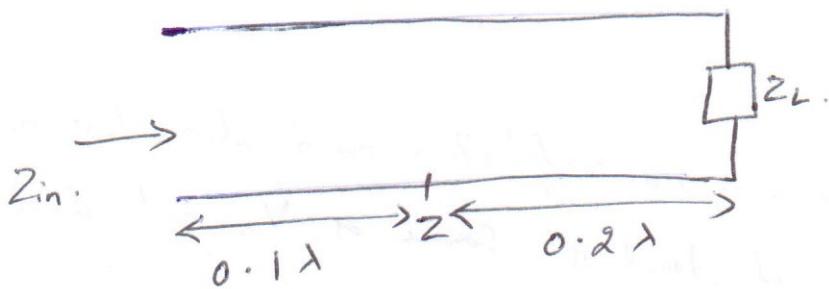
⑩ If 50Ω lossless line has $\Gamma = 0.5 \angle 300^\circ$ at a location z . what is the load Impedance and Input impedance, VSWR.



The Complete Smith Chart


Black Magic Design

2

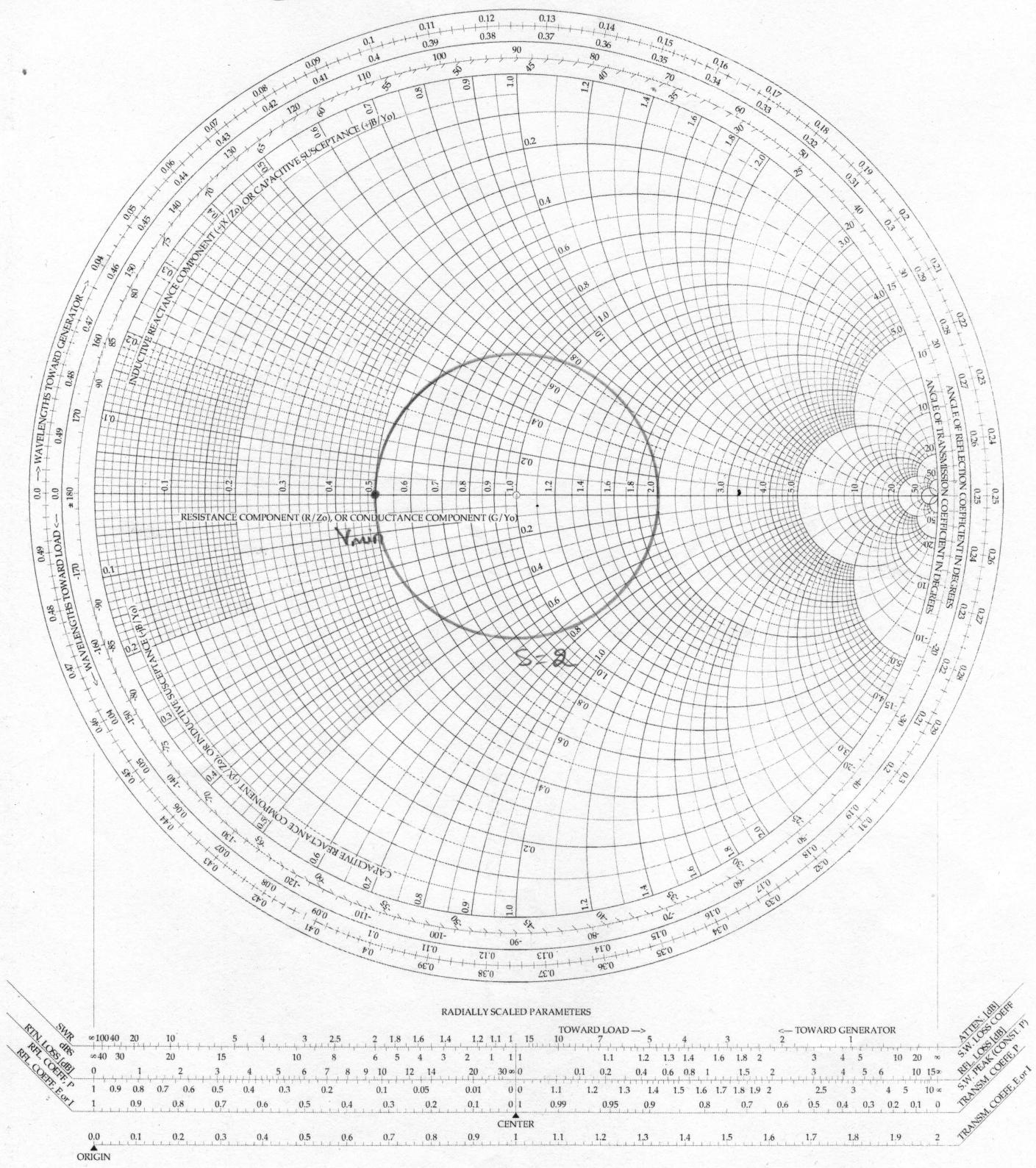


The Complete Smith Chart

Black Magic Design

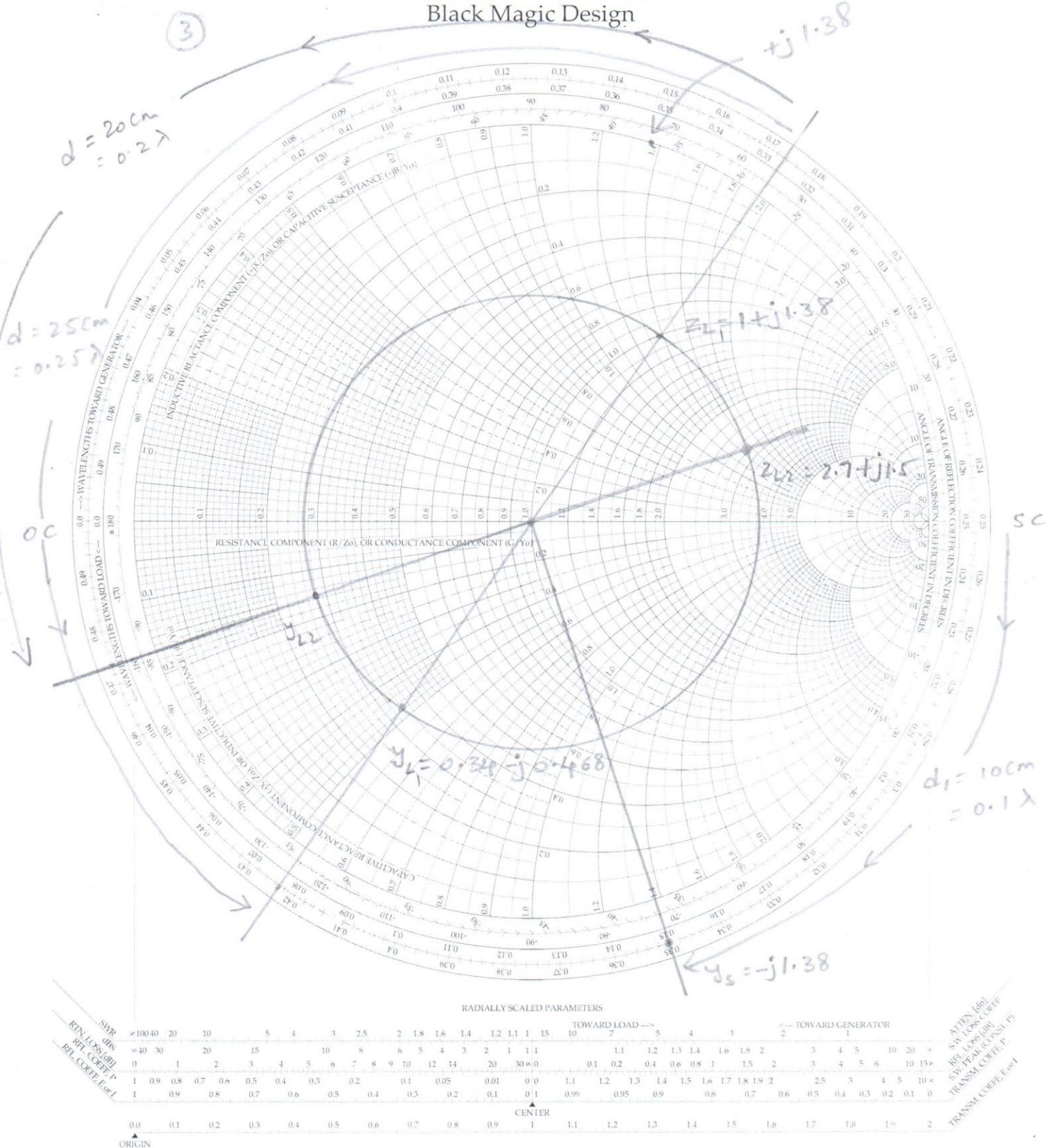

The Complete Smith Chart

Black Magic Design

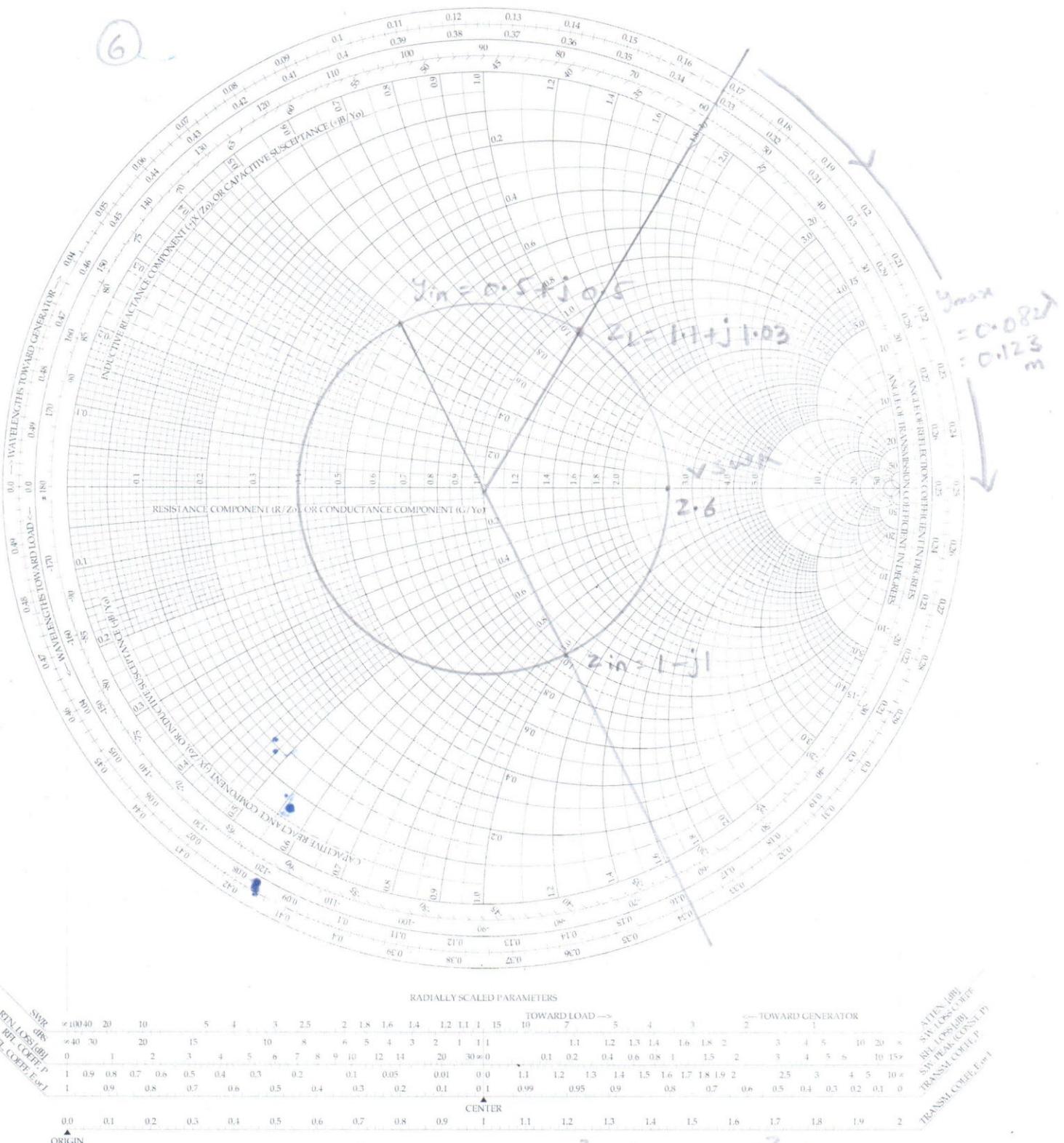


$$Y_{in} = (0.5 + j0.5) \frac{1}{200} = 0.25 \times 10^{-3} + j 0.25 \times 10^{-3} \Omega$$

$$Z_L = (1 + j1.03) 200 = 220 + j 206 \Omega$$

The Complete Smith Chart

Black Magic Design

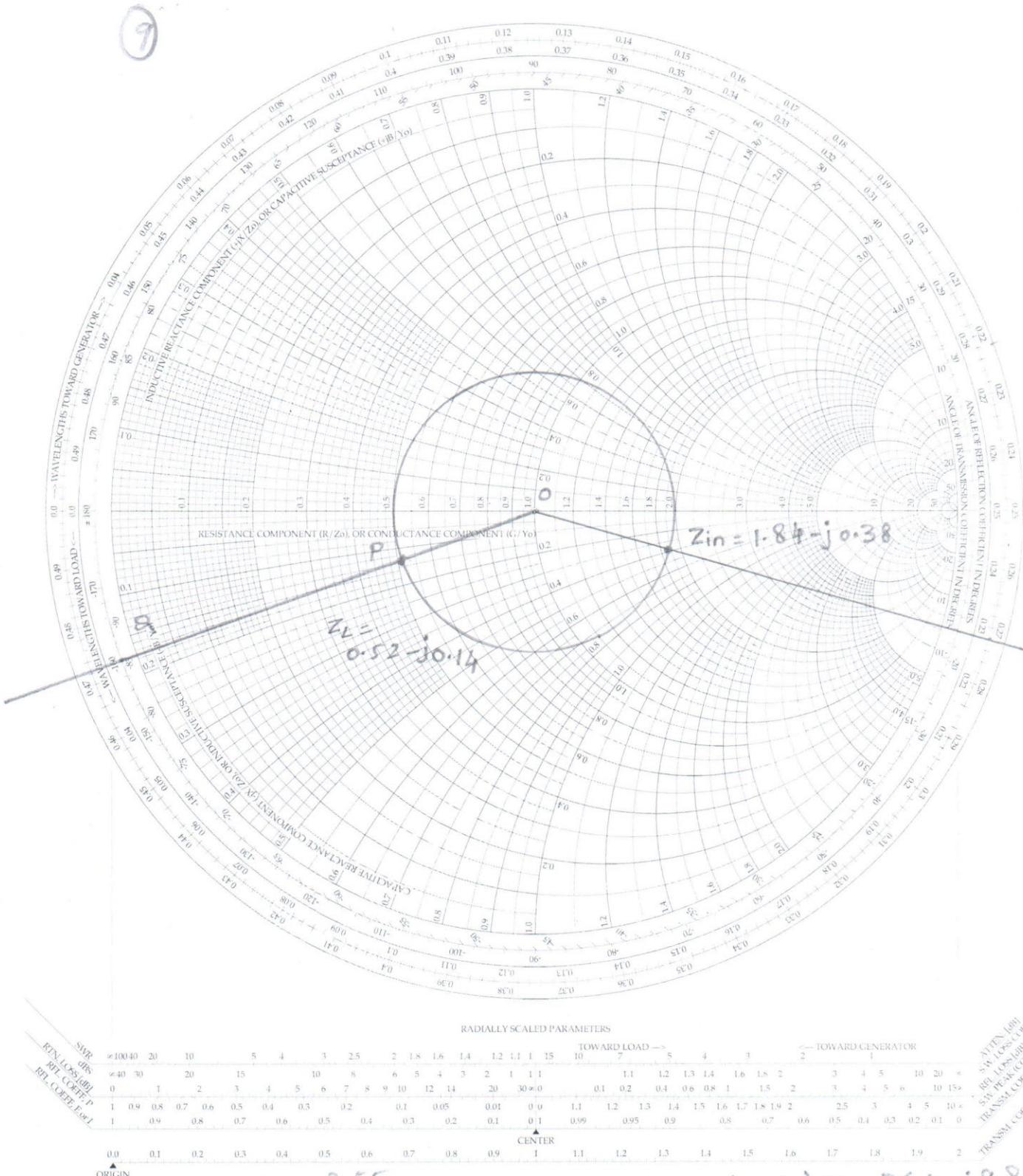

$$|\Gamma| = \frac{OP}{OA} = \frac{2.55}{7.6} = 0.33$$


$$\Gamma = 0.33 \angle 200^\circ$$

$$Z_L = (0.52 - j0.14) 70 = 36.4 - j9.8 \Omega$$

$$Z_{in} = (1.84 - j0.38) 70 = 128.8 - j26.6 \Omega$$

The Complete Smith Chart

Black Magic Design

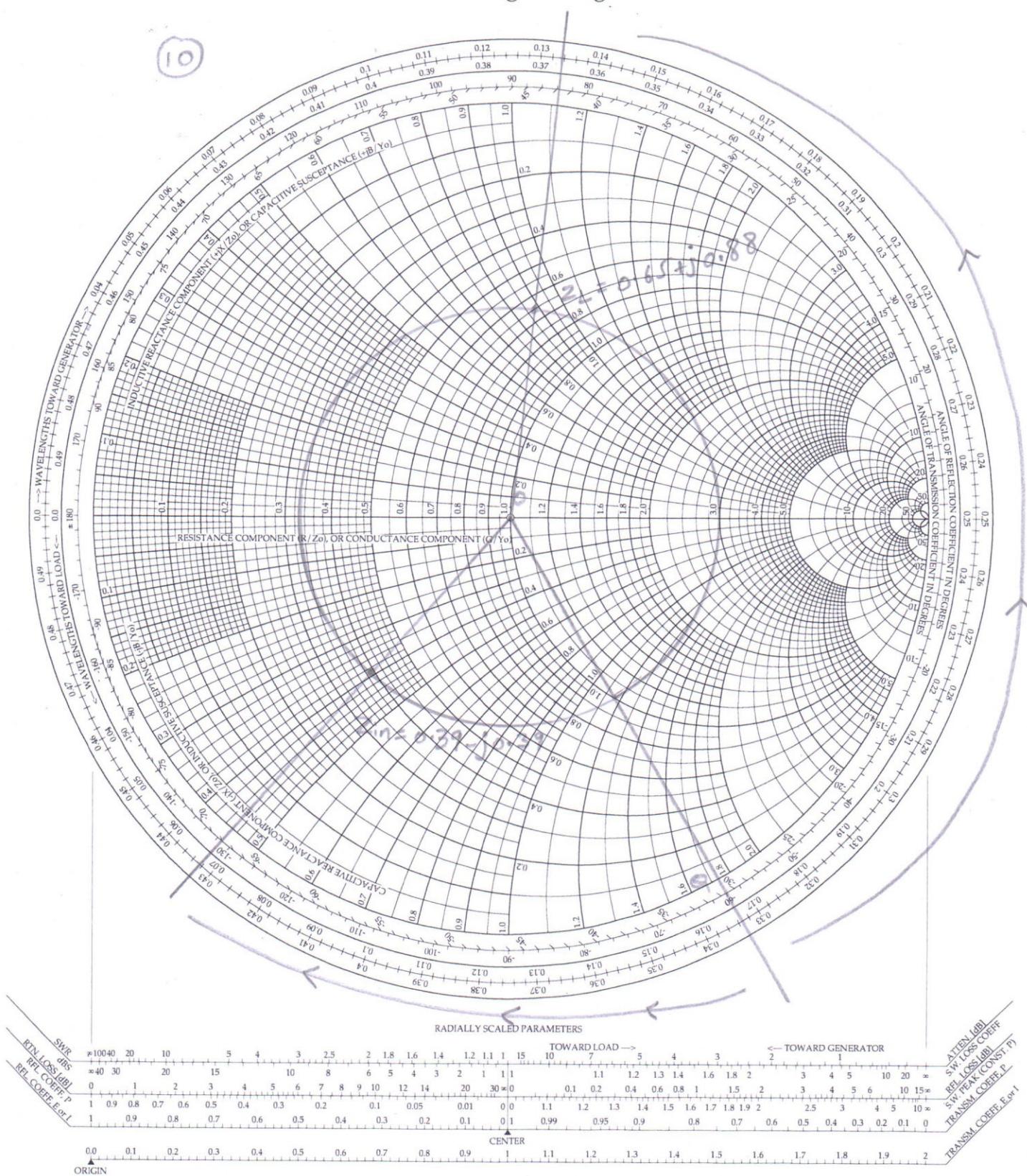

$$\frac{OP}{OQ} = 0.5 \Rightarrow OP = 0.5 \times 7.7 = 3.85 \quad VSWR = 3$$

$$Z_{in} = (0.39 - j0.39)50 = 19.5 - j19.5 \Omega$$

$$Z_L = (0.65 + j0.88)50 = 32.5 + j44 \Omega$$